avestão 01

a)
$$S_n = 2400 \times 20,833 = 49999,20 (50 kVA)$$

c) Perdas = $396 + 810 - 1206 W$

$$\eta = \frac{50000 - 1206}{50000} = 97,588\%$$

d)
$$R_p = \frac{120^2}{396} = 36,364 A (lado d BT)$$

$$I_P = \frac{120}{36,364} = 3,300 A$$
, $I_m = \sqrt{9,65^2 - 3,300^2} = 9,068 A$

e)
$$X_{m} = \frac{120}{9068} = 13,233 \Omega (lado de BT)$$

$$X_{\text{mat}} = 13,233 \times 400 = 5293,200 \Omega$$

a)
$$Z_{AT} = \frac{92}{20,833} = 4,416 \Omega$$
, $X = \sqrt{2^2_{AT}} - R_{AT}^2 = 4,002 \Omega$

Questão 02
$$P = 270W, P = \frac{270}{15000} = 0,018$$

$$R = \frac{1^{2}}{0,032} = 149,925 pu$$

$$R = \frac{1}{0,0667} = 149,925 pu$$

$$R = \frac{1}{149,925} = 0,00667 pu$$

$$R = \frac{1}{149,925} = 31,949 pu$$

$$Rp = \frac{1^2}{000667} = 149,925 pu$$

b)
$$I_p = \frac{V}{R_p} = \frac{1}{(49,925)} = 0,00667 \text{ pu}$$

$$I_m = \sqrt{I_p^2 - I_p^2} = \sqrt{0,032^2 - 0,00667} = 0,0313 \text{ pu}$$

$$X_m = \frac{1}{I_m} = \frac{1}{0,0313} = 31,949 \text{ pu}$$

$$e$$
 $M = \frac{1 - pendan}{1} = \frac{1 - 370/15000}{1} = 97,533\%$

f)
$$Im = 0.0313$$
 pu (calculado acima)
q) $V = 110^{\circ} + (0.018 + j0.01735) 1 / 25.842 = 110 + 0.0250 / 43.947.1 / 25.842 = 1 + 0.025 / 69.789 = 1 + 0.025$

Questão 03

As perdes foro se mantem aproximada mente constantes nusuro variando a carga, Dessa forma Por éconstante. Na condição de plena carga as perdas no cobre são: Paul = RI2

Na condição de 50% de carga as perdas cobre serão:

Questão 04

$$V_{f} = 7967,434 + (68,028 + j84,898) 1,883 [-36,878] = 7967,434 + 108,791 [51,295,1,883] -36,878 = 8165,988 = 14143,906 V
b) $R = \frac{14143,966 - 13800}{13800} = 2,492\%$$$